

## 80m CW transceiver

Written by Hans Summers

Saturday, 21 November 2009 23:13 - Last Updated Saturday, 21 November 2009 23:51

---

### 80m CW Tranceiver by [Raimo Jarvi](#) OH8MNM, Finland

Raimo's crystal-controlled QRP tranciever provides 1-2 W of output using 2 transistors in the transmitter. The receiver section contains two FET's and an LM741 IC for the audio. and a crystal.

{gallery}gallery2{/gallery}